
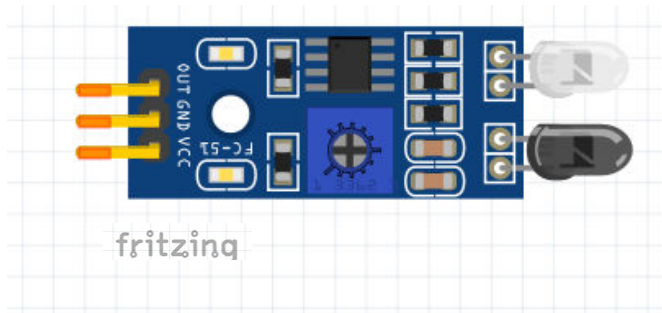


Self-Driving Car build sheet

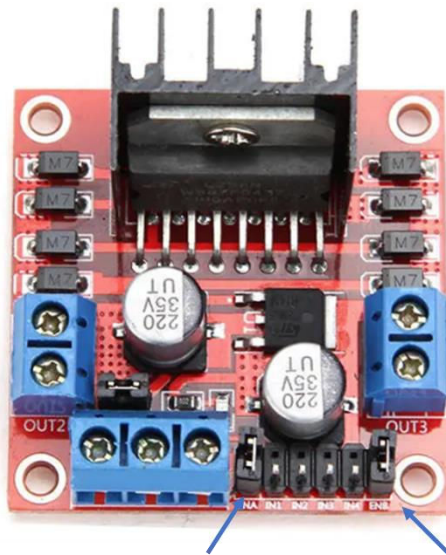

Left infra-red sensor		
Pin	Wire Colour	Connects to
OUT		6
VCC		7
GND		8



ENA IN1 IN2 IN3 IN4 ENB

Motor drive board		
Pin	Wire Colour	Connects to
ENA		9
IN1		2
IN2		3
IN3		4
IN4		5
ENB		10